

EC413 Discussion 9 Lab 7

Xiteng Yao

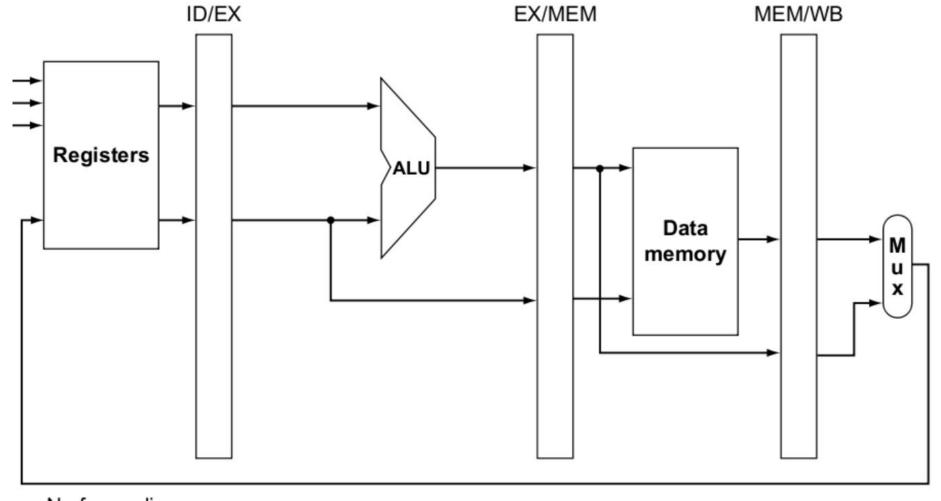

a. No forwarding

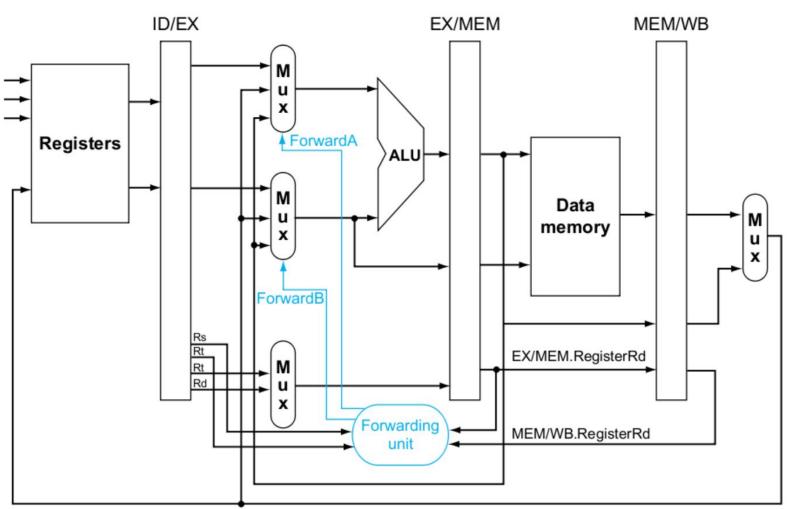


1 Ahead Forwarding

Implement a forwarding unit module

Checks if there is a regwrite at EX/MEM and check if the dest is Rs/Rt

If yes, forward output as input

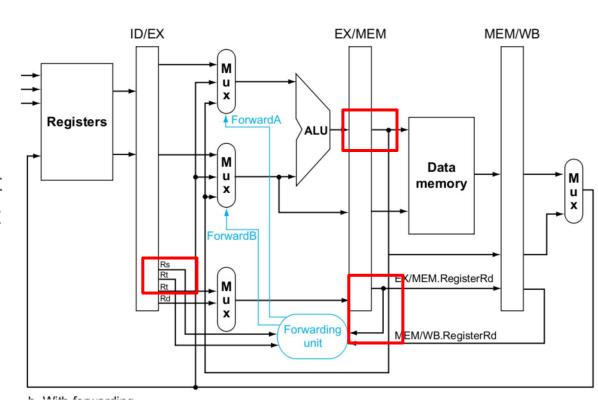


2 Ahead Forwarding

Similarly, add logics to the forwarding module

Now instead of checking the EX/MEM. Checks the MEM/WB stage.

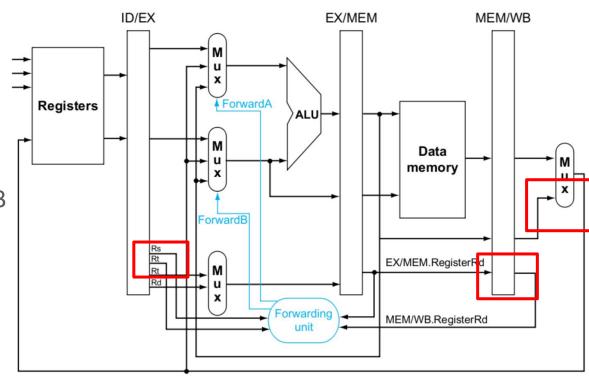Make sure that 1 and 2 ahead forwarding logics do not have any conflict.



Arbitration, \$0 write logic, and No write

- Examine the logic in the forwarding unit so that it selects from the
 1 and 2 ahead forwarding correctly
 - 1 ahead has higher priority
 - If no regwrite in 1 ahead, check 2 ahead
 - If neither has regwrite, read from register normally
- \$0 is a special register
 - It is always 0
 - So read and write of this register shall also be considered in the forwarding unit

Summary

You need to implement a forwarding unit and 2 muxes

Connect them to different signals in the CPU module

Example logic shown below, just for understanding, don't copy it

```
ForwardA = ForwardB = 00 //initialize

IF (EX/MEM.RegWrite && EX/MEM.RegisterRd ~= 0 &&
        EX/MEM.RegisterRd == ID/EX.RegisterRs) ForwardA = 10

IF (EX/MEM.RegWrite && EX/MEM.RegisterRd ~= 0 &&
        EX/MEM.RegisterRd == ID/EX.RegisterRt) ForwardB = 10

IF (MEM/WB.RegWrite && MEM/WB.RegisterRd ~= 0 &&
        EX/MEM.RegisterRd ~= ID/EX.RegisterRs &&
        MEM/WB.RegisterRd == ID/EX.RegisterRs) ForwardA = 01
```

MEM/WB.RegisterRd == ID/EX.RegisterRt) ForwardB = 01


IF (MEM/WB.RegWrite && MEM/WB.RegisterRd ~= 0 &&

EX/MEM.RegisterRd ~= ID/EX.RegisterRt &&

```
ID/EX
                                            EX/MEM
                                                                   MEM/WB
                           Forward
Registers
                                       ALU
                                                          Data
                                                        memory
                                                     EX/MEM.RegisterRd
                                    Forwarding
                                                     MEM/WB.RegisterRd
```

EC: LW after SW

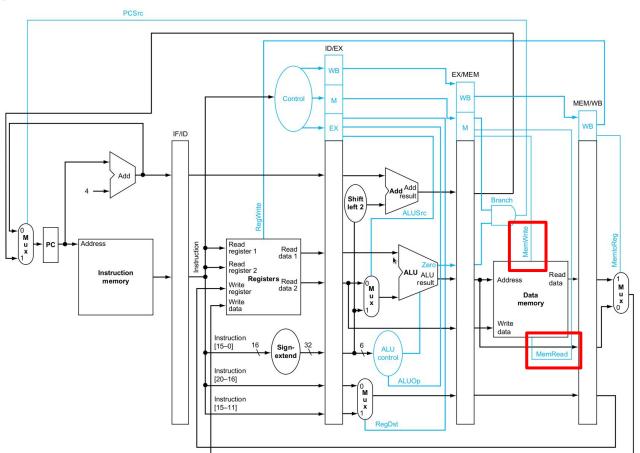- Add a similar
 Memory
 Forwarding unit
- Check memread and memwrite signal and forward as needed
- No stall needed



Extra EC opportunities - 10 points

Participate an experiment of using Github CI/CD for grading this lab

Sign up here

Need to commit and push to Github during completion of the lab and provide feedbacks

Limited availability, depending on my progress and feedback

Invitations will be out on Tuesday